

Registration No.:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

Course: B.Tech/IDD  
Sub\_Code: EOPC2002

3<sup>rd</sup> Semester Regular/Back Examination: 2025-26

SUBJECT: Analog and Digital Electronic Circuits

BRANCH(S): EE, BIOMED, EEE, ELECTRICAL, ELECTRICAL & C.E, ELECTRONICS & C. E

Time: 3 Hours

Max Marks: 100

Q.Code: U558

Answer Q1 (Part-I) which is compulsory, any eight from Part-II, and any two from Part-III.  
The figures in the right-hand margin indicate marks.

### Part-I


Q1 Answer the following questions: (2 x 10)

- What is load line? Why this is straight line?
- What is a model? Obtain the  $r_e$  model of all the three configurations of BJT.
- Draw and explain the fixed bias configuration using a P-channel depletion type MOSFET.
- Draw the equivalent model of JFET voltage divider configuration and find its  $Z_i$  and  $Z_o$ .
- Explain the Wien-Bridge oscillator circuit.
- How class B amplifier is different from class A amplifier?
- Simplify the Boolean expression  $Y = \sum m(2, 4, 6)$ .
- Derive the K-maps and simplified expressions for outputs of a half adder.
- Differentiate between a combinational circuit and a sequential circuit.
- How registers are designed? How can you classify registers? Explain.

### Part-II

 
Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- Explain the operation of voltage divider biasing using BJT. Why is it widely used?
- For the network of figure given below,
  - Find  $Z_i$ ,  $Z_o$ ,  $A_v$ , and  $A_i$  with  $r_e = \infty$ .
  - Repeat (I) with  $r_e = 50 \Omega$ .




- For a voltage feedback biasing circuit with  $\beta = 45$ ,  $V_{CC} = 24 \text{ V}$ ,  $V_{CE} = 5 \text{ V}$ ,  $R_C = 10 \text{ k}\Omega$ , and  $R_E = 270 \Omega$ , find the value of feedback resistance  $R$ .
- Explain the self-bias configuration of FET biasing. Discuss about its stability.

 - e) Draw the small signal equivalent model of a common source amplifier circuit using N-Channel D-MOSFET and find its necessary parameters  $Z_i$ ,  $Z_o$ ,  $A_v$ , and  $A_i$
- f) Determine the value of  $Z_i$ ,  $Z_o$ ,  $A_v$ , and  $A_i$  for the given circuit with  $I_{DSS} = 6 \text{ mA}$ ,  $V_P = 6 \text{ V}$ , and  $R_d = 40 \text{ K}\Omega$



 - g) Write the Bark-Hausen's criteria for oscillation. Explain the working principle of an oscillator.
- h) Explain the RC-Phase shift oscillator and find the expression for the frequency of oscillation.
- i) Use the Quine-McCluskey method of minimization and find the expression for  $f(A, B, C, D) = \sum m(2, 4, 8, 11, 15) + d(1, 10, 12, 13)$
- j) Implement a full adder using 8:1 multiplexer.
- k) Explain the working operation of a D-flip flop.
- l) Consider the given circuit shown below. Here the initial output condition is  $Q_A Q_B Q_C = 010$ . Write the truth table of output  $Q_A Q_B Q_C$  for 4 clock pulses.



**Part-III**

**Only Long Answer Type Questions (Answer Any Two out of Four)**

- Q3** Discuss all about the compound configurations of cascade, cascode, Darlington, and current mirror circuits (16)
- Q4** Find the parameters  $Z_i$ ,  $Z_o$ ,  $A_v$ , and  $A_i$  of Common gate and source follower amplifiers. (16)
- Q5** What is a power amplifier? How is it classified? Explain the operation of push-pull amplifier circuit. Find the efficiency of class-B amplifier and compare it with that of class-A amplifier (16)
- Q6** Write a note on one bit magnitude comparator. Design a ripple counter for the state diagram shown in figure below. (16)

