

Registration No.:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

Course: B.Tech/IDD
Sub_Code: 23ES1002

1st Semester Regular/Back Examination: 2025-26

SUBJECT: BASIC ELECTRONICS

BRANCH(S): AE, AEIE, AERO, AIML, AUTO, BIOTECH, CHEM, CIVIL, CS, CSE, CSEAI, CSEAIML, CSEDS, CSIT, CST, ECE, EEE, EEVDT, ELECTRICAL, ELECTRICAL & C.E, ELECTRONICS & C.E, ETC, IT, MECH, METTA, MINERAL, MINING, MME

Time: 3 Hours

Max Marks: 100

Q.Code: U728

Answer Q1 (Part-I) which is compulsory, any eight from Part-II, and any two from Part-III.
The figures in the right-hand margin indicate marks.

Part-I

Q1 Answer the following questions: (2 x 10)

- Mention few properties of semiconductor.
- What do you understand by depletion region? How it is formed in a diode?
- Define leakage current in CB configuration.
- Compare between a BJT and a JFET.
- What type of gate voltage is necessary in an n-channel D-MOSFET and n-channel E-MOSFET to cause current flow?
- What is the significance of the term "monolithic IC"?
- Define slew rate in connection with an OP-AMP.
- Add the binary numbers 10111 and 111.
- Represent $(-5)_{10}$ in sign magnitude and 1's complement form.
- Implement NOT using NAND.

Part-II

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- For a transistor, $I_c = 7 \text{ mA}$, $I_{CO} = 25 \mu\text{A}$ and $I_B = 0.1 \text{ mA}$. Calculate α , β , and I_E .
- Draw the CB output characteristics of a transistor. Answer the followings.
 - Indicate all region of operation
 - mention biasing and current expressions
- With neat sketch, describe the operation of a center-tapped FWR.
- The reverse saturation current at 300 K of a p-n junction Ge diode is $5 \mu\text{A}$. Find the voltage to be applied across the junction to obtain a forward current of 50 mA.
- Mention the relationship between V_{GS} , V_P , and $V_{D,Sat}$. An n-channel JFET has the following parameters: $I_{DSS} = 10 \text{ mA}$ and $V_P = -4\text{V}$. If $V_{GS} = -2.5 \text{ V}$, find the drain current?
- State the limitations of integrated circuits.

- g) Mention characteristics of ideal OP-AMP. Discuss the concept of virtual ground in OP-AMP circuits and explain its significance in circuit analysis.
- h) Is negative feedback reducing the gain of an amplifier? Justify your answer with suitable block diagram.
- i) Convert the followings:
 i) $(FACE)_{16} = (?)_{10}$
 ii) $(15.45)_{10} = (?)_2$
 iii) $(101011011011.1101)_2 = (?)_8$
- j) Simplify the following Boolean expressions.
 (i) $Y(A, B, C, D) = A\bar{C} + \bar{B}D + \bar{A}CD + ABCD$
 (ii) $Y(A, B, C) = (\bar{A} + \bar{B})(\bar{A} + \bar{C})(\bar{B} + \bar{C})$
- k) Differentiate between conventional CRO and DSO.
- l) What is amplitude modulation? Obtain an expression for an AM wave with sinusoidal modulation.

Part-III

Only Long Answer Type Questions (Answer Any Two out of Four)

- Q3 Describe the forward bias and reverse bias operation of p-n junction diode using suitable diagrams. Draw the characteristics curve. (16)
- Q4 With a neat sketch, explain the construction and principle of operation of p-channel D-MOSFET. (16)
- Q5 With suitable diagram, describe the use of an OP-AMP as subtractor. (16)
- Q6 Draw the block diagram of a DSO. Explain the function of each block. (16)