

Registration No.:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

Course: Integrated Dual Degree (B.Tech and M.Tech)
Sub_Code: REL4C001/ REE4C001/RBM4C001

4th Semester Regular/Back Examination: 2023-24

SUBJECT: DIGITAL ELECTRONICS

BRANCH(S): ELECTRICAL, EE, EEE, BIOMED

Time : 3 Hour

Max Marks : 100

Q.Code: P056

Answer Question No.1 (Part-1) which is compulsory, any eight from Part-II and any two from Part-III.

The figures in the right hand margin indicate marks.

Part-I

Q1 Answer the following questions :

(2 x 10)

- Find out the hexadecimal equivalent of $(707.77)_8$.
- Write down any two applications of EX-OR gate.
- What will be $a \oplus b$, if $ab = 0$?
- How many 3 to 8 line decoders with an enable input are needed to construct a 6 to 64 line decoder without using any other logic gates?
- Write the difference between synchronous inputs and asynchronous inputs.
- The output of a J-K flip-flop is 0. Its output does not change when a clock pulse is applied. What can be the inputs J and K respectively?
- What is ALU?
- Differentiate between PLA & PAL.
- What is sequential circuit? Also draw a 1-bit memory circuit.
- What is FPGA?

Part-II

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve)

(6 x 8)

- Implement EX-OR gate using minimum number of NAND gates.
- Obtain the simplified form for the given maxterm expression using K-map.
 $f(A, B, C, D) = \prod(0,1,4,5,6,7,9,14) \cdot d(13,15)$
- Implement the given functions using single 3:8 decoder.
 $f_1(A, B, C) = \prod(2,3,4,5,7)$
 $f_2(A, B, C) = \sum(1,3,5)$
- Illustrate CCD memory and write its few applications.
- Explain any one of the error detecting & error correcting coding scheme.
- Explain Mod-5 ripple counter using JK-FF with its output wave forms.
- Explain operation of 4-bit SIPO with necessary diagram.
- Write down the specifications for D/A converter and also explain it.


- i) Design a magnitude comparator to compare two 3-bit binary numbers.
- j) Give an example of A/D converter and mention its few important characteristics.
- k) Design S-R flip-flop to D flip-flop conversion. Find the conversion table.
- l) Explain the operation of TTL with required diagram.

Part-III

Only Long Answer Type Questions (Answer Any Two out of Four)

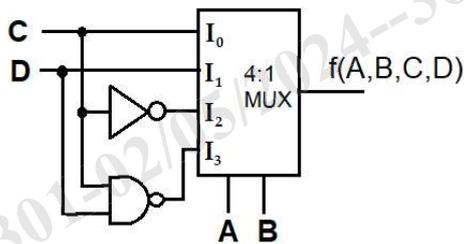- Q3 a)** Simplify the given function using K-map. Also find its POS result. **(8+8)**
 $f(A, B, C) = \sum m(0, 2, 4, 6, 7, 8, 10, 12, 13, 15)$

- b)** Find the Boolean function implemented in the figure using 4:1 MUX.



- Q4 a)** Design a BCD adder with proper explanation. **(8+8)**
b) Discuss the working of CMOS circuit as a digital logic operation.

- Q5** Design a decade counter using T-FF. Also draw its waveforms. **(16)**

- Q6 a)** Explain the design principle of ROM. Mention its differences than RAM. **(8+8)**
b) Explain A/D converter using voltage-to-frequency conversion with proper circuit and waveforms.