

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech
RBM4C001/REE4C001/REL4C001

4th Semester Regular/Back Examination: 2023

SUBJECT: Digital Electronics

BRANCH(S): BIOMED, EEE, ELECTRICAL

Time : 3 Hour

Max Marks : 100

Q.Code : M217

Answer Question No.1 (Part-1) which is compulsory, any eight from Part-II and any two from Part-III.

The figures in the right hand margin indicate marks.

Part-I

Q1 Answer the following questions:

(2 x 10)

- Write the binary equivalent of $(101.11)_8$
- What is the importance of Priority encoder?
- Draw CMOS logic circuit & write its one application.
- What is the specialty of EX-OR gate?
- Compare synchronous counter with asynchronous counter.
- What is the minimum number of flip-flops needed to design a mod-16 counter?
- Define PLA & PAL.
- Write some applications of MUX & DMUX.
- How JK Flipflop is converted to T-Flipflop?
- What is FPGA?

Part-II

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- Draw TTL circuit & explain its operation.
- Draw the truth table & circuit for full Adder. Also mention its output equations.
- Implement the given functions using single 3:8 decoder.

$$f_1(A, B, C) = \prod(2, 3, 4, 5, 7)$$

$$f_2(A, B, C) = \sum(1, 3, 5)$$

- Do a conversion of SR-FF to D-FF with detailed truth table & K-Map analysis.
- Discuss any two error detecting codes & also any two correcting codes with examples.

- f) Design a 2-bit synchronous up counter.
- g) Write down two applications of each for MUX, Flipflop, Counter, Ex-OR gate, shift register & CMOS.
- h) Simplify the expression using K-maps: $F(x, y, z) = \pi(0,2,4,5,7)$
- i) Explain operation of ring counter with suitable output wave diagram.
- j) The initial contents of the 4-bit serial in parallel out shift register is 1011. What will be contents of the given shift register after 5 clock pulses applied?
- k) Explain operation of successive approximation A/D converter.
- l) Draw a ROM structure & discuss its function.

Part-III

Only Long Answer Type Questions (Answer Any Two out of Four)

- Q3** a) Discuss operation of the carry look ahead adder with the proper logic flows. (8)
- b) Obtain the simplified form for the given expression using K-map. (8)
- Also, draw the minimization result using NAND gate only.
- $F(A, B, C, D) = \Sigma m(1, 3, 4, 6, 8, 9, 11, 13, 15) + \Sigma d(0, 2, 14)$
- Q4** a) A majority circuit is a combinational circuit whose output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise. Design a 3 input majority circuit. (8)
- b) Find the Boolean function for 8:1 MUX. (8)
- Q5** a) Design a decade counter by using JK-FF or T-FF. (8)
- b) Explain shifting of data in serial left & serial right manner with suitable logic circuits. (8)
- Q6** a) How analog to digital conversion happens, Show it stepwise. (8)
- b) Explain PLD & CPLD. (8)