

Registration No.:

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

Total Number of Pages: 02

Course: B.Tech  
Sub\_Code: REI4C001

4<sup>th</sup> Semester Regular/Back Examination: 2023-24  
SUBJECT: Electrical & Electronics Measurement  
BRANCH(S): AEIE, EIE  
Time: 3 Hours  
Max Marks: 100  
Q.Code: P588

Answer Question No.1 (Part-1) which is compulsory, any eight from Part-II and any two from Part-III.

The figures in the right hand margin indicate marks.

**Part-I**

**Q1 Answer the following questions: (2 x 10)**

- Give some examples of units of measurement in the International System of units.
- State any two benefits of electronic energy meter.
- When bridge is used in measurement and why?
- How the capacitance measured for a capacitor?
- What are galvanometer constants?
- Define logarithmic decrement and what its unit is.
- Distinguish between PT & CT.
- Give reasons, the secondary of a CT is never left open circuited.
- Explain the parts of a typical CRO.
- How you can measure phase angle in a CRO.

**Part-II**

**Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)**

- Explain the concept and rules of significant figures in measurements.
- Explain the working of PMMI meter with neat sketch.
- What is Maxwell's bridge? Derive the equation of balance for the bridge.
- Explain Wagner earthing device.
- Describe the process of calibrating a Galvanometer.
- Describe magnetic flux. What are the units of magnetic flux? How are they derived?
- List out different AC voltmeters and explain the working of any one of them.
- Discuss the working principle of Q-meter and its applications.
- Distinguish between CRO and DSO.
- Draw the block diagram of delay line circuit and explain its working.
- Describe the construction of dynamometer type single phase wattmeter.
- Describe a true rms reading voltmeter with neat sketches.

**Part-III**

**Only Long Answer Type Questions (Answer Any Two out of Four)**

- Q3** a) Explain the procedure how to find different errors in measurement with rectification. (8)  
b) What are the errors in electro-dynamometer type watt meters? Explain them. (8)
- Q4** a) Derive equation of balance for an Anderson's bridge. Draw phasor diagram for conditions under balance. (8)  
b) Explain the working principle of Wagner earthing device. (8)
- Q5** a) Explain the construction and theory of operation of DC potentiometers. (Any one) (8)  
b) Describe the working of Ballistic Galvanometer and compare it with D'Arsonval Galvanometer. (8)
- Q6** a) Explain construction and working of DSO in detail. (8)  
b) Draw a neat block diagram of a Cathode Ray Oscilloscope and specify the function of each block. Also explain its working principle. (8)